



Name _____ Class _____ Date _____

1


A 10-ohm resistor and a 20-ohm resistor are connected in series to a voltage source. When the **current** through the 10-ohm resistor is **2.0 amperes**, what is the **current** through the 20-ohm resistor?

- A 1.0 A
- B 2.0 A
- C 0.50 A
- D 4.0 A

2

What is the **total resistance** of the circuit segment shown in the diagram below?

- A 1.0 Ω
- B 9.0 Ω
- C 3.0 Ω
- D 27 Ω

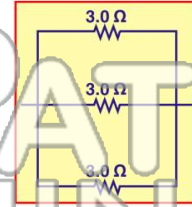

3

A **12.0-meter** length of copper wire has a resistance of **1.50 ohms**. How **long** must an **aluminum wire** with the same cross-sectional area be to have the **same**

4

What is the **total current** in a circuit consisting of **six operating 100-watt lamps** connected in parallel to a **120-volt source**?

5



PREVIEW

Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet


7

What is the **resistance** of **each** resistor?

- A 20 Ω
- B 40 Ω
- C 80 Ω
- D 160 Ω

current. The **resistance** of the heater is

- A 0.018 Ω
- B 28 Ω
- C 55 Ω
- D 220 Ω

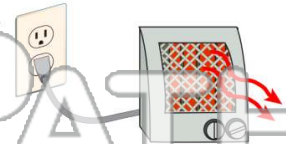

9

A **10-meter** length of wire with a cross-sectional area of 3.0×10^{-6} square meter has a resistance of 9.4×10^{-2} ohm at **20° Celsius**. The wire is most likely **made of**

- A silver
- B copper
- C aluminum
- D tungsten

10

A **potential drop of 50 volts** is measured across a **250-ohm resistor**. What is the **power** developed in the resistor?

- A 0.20 W
- B 5.0 W
- C 10 W
- D 50 W




Name _____ Class _____ Date _____

1 A 10-ohm resistor and a 20-ohm resistor are connected in series to a voltage source. When the **current** through the 10-ohm resistor is **2.0 amperes**, what is the **current** through the 20-ohm resistor?

- A 1.0 A
- B 2.0 A
- C 0.50 A
- D 4.0 A

2 What is the **total resistance** of the circuit segment shown in the diagram below?

- A 1.0 Ω
- B 9.0 Ω
- C 3.0 Ω
- D 27 Ω

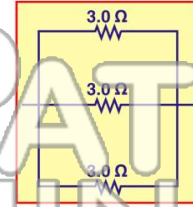

3 A **12.0-meter** length of copper wire has a resistance of **1.50 ohms**. How **long** must an **aluminum** wire with the same cross-sectional area be to have the **same**

4 What is the **total current** in a circuit consisting of **six operating 100-watt lamps** connected in parallel to a **120-volt** source?

PREVIEW


Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet

7 What is the **resistance** of **each** resistor?

- A 20 Ω
- B 40 Ω
- C 80 Ω
- D 160 Ω

current. The **resistance** of the heater is

- A 0.018 Ω
- B 28 Ω
- C 55 Ω
- D 220 Ω

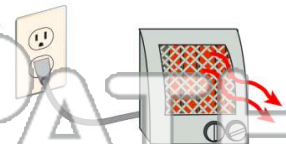

9 A **10-meter** length of wire with a cross-sectional area of 3.0×10^{-6} square meter has a resistance of 9.4×10^{-2} ohm at **20° Celsius**. The wire is most likely **made of**

- A silver
- B copper
- C aluminum
- D tungsten

10 A **potential drop of 50 volts** is measured across a **250-ohm** resistor. What is the **power** developed in the resistor?

- A 0.20 W
- B 5.0 W
- C 10 W
- D 50 W