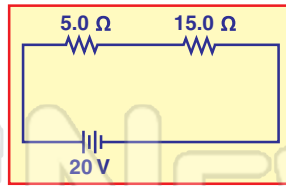




Name _____ Class _____ Date _____

1 The diagram below shows two resistors connected in series to a 20-volt battery. If the current through the 5.0-ohm resistor is 1.0 ampere, the current through the 15.0-ohm resistor is _____.


Circle the answer.




- 1.0 A 0.33 A 1.3 A 3.0 A

6 How much current flows through a 12-ohm flashlight bulb operating at 3.0 volts?

- 0.25 A 3.0 A
0.75 A 4.0 A

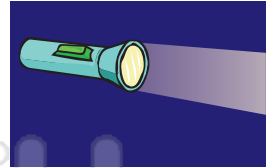

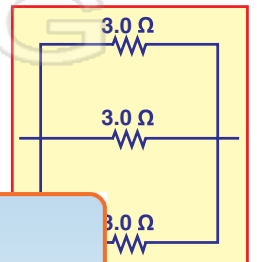7 What is the total resistance of the circuit segment shown in the diagram? Write the answer.



2 The diagram below represents an electric circuit. What is the total amount of energy delivered to the resistor in _____.

4.0 V



PREVIEW

Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet

4 If a 30-ohm resistor is connected in parallel with a 30-ohm resistor, the equivalent resistance is _____.

- 2.0 Ω 10 Ω 15 Ω 45 Ω

- a. 1.7×10^{-4} A
b. 2.4×10^{-2} A
c. 6.0×10^3 A




5 A 10-meter length of wire with a cross-sectional area of 3.0×10^{-6} square meter has a resistance of 9.4×10^{-2} ohm at 20°C. The wire is most likely made of _____.

- silver copper aluminum



10 A current of 3.0 amperes is flowing in a circuit. How much charge passes a given point in the circuit in 30 seconds?

- 0.10 C 33 C
10 C 90 C

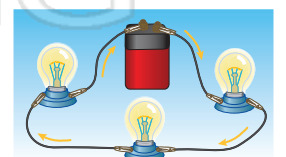




Electric Circuits - Answer Key

H.S. Phys

Name _____ Class _____ Date _____

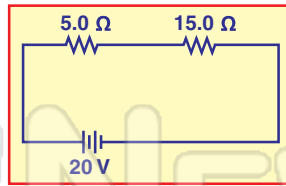
- 1 The diagram below shows two resistors connected in series to a 20-volt battery. If the current through the 5.0-ohm resistor is 1.0 ampere, the current through the 15.0-ohm resistor is _____.
- Circle the answer.




1.0 A 0.33 A 1.3 A 3.0 A

- 6 How much current flows through a 12-ohm flashlight bulb operating at 3.0 volts?

0.25 A 3.0 A
0.75 A 4.0 A

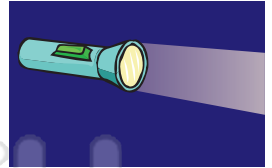

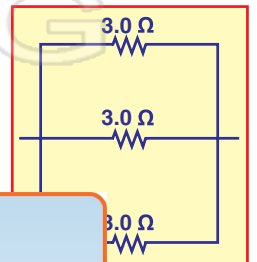- 7 What is the total resistance of the circuit segment shown in the diagram? Write the answer.



1.0 Ω

- 2 The diagram below represents an electric circuit. What is the total amount of energy delivered to the resistor in _____.

4.0 V



PREVIEW

Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet

- 4 If _____ with a 30-ohm resistor, the equivalent resistance is _____.

2.0 Ω 10 Ω 15 Ω 45 Ω

a. 1.7×10^{-4} A
b. 2.4×10^{-2} A
c. 6.0×10^3 A



- 5 A 10-meter length of wire with a cross-sectional area of 3.0×10^{-6} square meter has a resistance of 9.4×10^{-2} ohm at 20°C. The wire is most likely made of _____.

silver copper aluminum



- 10 A current of 3.0 amperes is flowing in a circuit. How much charge passes a given point in the circuit in 30 seconds?

0.10 C 33 C
10 C 90 C

