

Lab Investigations



Date Name_ Class A 20-ohm resistor and a 30-ohm resistor A 20-ohm resistor and a 30-ohm resistor are connected in parallel to a 12-volt battery are connected in parallel to a 12-volt battery as shown. An ammeter is connected as shown. as shown. An ammeter is connected as shown. What is the equivalent resistance What is the current reading of the ammeter? of the circuit ABCD 10 Ω B 0.60 A 12Ω C 0.40 A ₹20Ω $\leq 30\Omega$ D 0.20 A A 20-ohm resistor and a 30-ohm resistor 3 Which physical quantity is correctly are connected in parallel to a 12-volt battery paired with its unit? as shown. An ammeter is connected as shown. 5 **PREVIEW** Please Sign In or Sign Up to download the printable version of this worksheet 7 A 10-1 m A energy B 100 m **B** power C momentum 101 m velocity **D** 10² m 9 A joule is equivale he weigh nearly equal to A N·m A 10-3 N B N·s B 10-2 N C N/m C 100 N D N/s D 10² N



Lab Investigations



Date Name_ Class A 20-ohm resistor and a 30-ohm resistor A 20-ohm resistor and a 30-ohm resistor are connected in parallel to a 12-volt battery are connected in parallel to a 12-volt battery as shown. An ammeter is connected as shown. as shown. An ammeter is connected as shown. What is the equivalent resistance What is the current reading of the ammeter? of the circuit B ABCD 10 Ω B 0.60 A 12Ω C 0.40 A ₹20Ω $\leq 30\Omega$ D 0.20 A A 20-ohm resistor and a 30-ohm resistor 3 4 Which physical quantity is correctly are connected in parallel to a 12-volt battery paired with its unit? as shown. An ammeter is connected as shown. D 5 **PREVIEW** A Please Sign In or Sign Up to download the printable version of this worksheet 7 A 10-1 m A energy B B 100 m **B** power C momentum 101 m velocity **D** 10² m 9 A joule is equivalent to he weigh nearly equal to A N·m A 10-3 N B Nes B 10-2 N C N/m C 100 N D N/s D 10² N