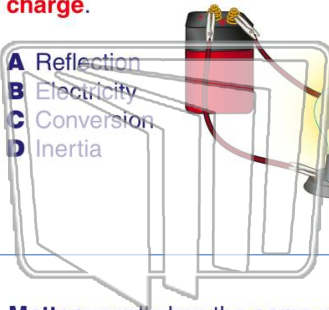




Name \_\_\_\_\_ Class \_\_\_\_\_ Date \_\_\_\_\_


1 \_\_\_\_\_ is the **flow of electrical charge**.

- A Reflection
- B Electricity
- C Conversion
- D Inertia



2 \_\_\_\_\_ are made of **three different particles**. Some have a positive charge, some have a negative charge, and some have no charge at all.

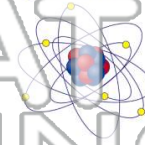- A Gases
- B Liquids
- C Solids
- D Atoms



3 **Matter** usually has the **same** number of positive and negative charges, making it **neutral**. If something had a charge of **-5**,

4 The **imbalance** of positive or negative charges **between** objects is called \_\_\_\_\_.




## PREVIEW

Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet

7 \_\_\_\_\_ purpose of the **battery**?

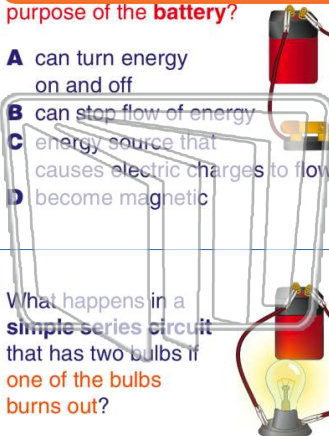- A can turn energy on and off
- B can stop flow of energy
- C energy source that causes electric charges to flow
- D become magnetic




8 \_\_\_\_\_ charge flows \_\_\_\_\_.

- A in two paths
- B in only one path
- C faster than parallel
- D backwards



9 What happens in a **simple series circuit** that has two bulbs if **one of the bulbs burns out**?

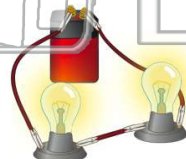- A the other bulb will burn dimmer
- B the other bulb will burn brighter
- C the other bulb will stay lit
- D the other bulb will go out too



10 A(n) \_\_\_\_\_ circuit has **two or more paths** the electric charge can flow through.

- A parallel
- B series
- C open
- D closed






Name \_\_\_\_\_ Class \_\_\_\_\_ Date \_\_\_\_\_


1 \_\_\_\_\_ is the **flow of electrical charge**.

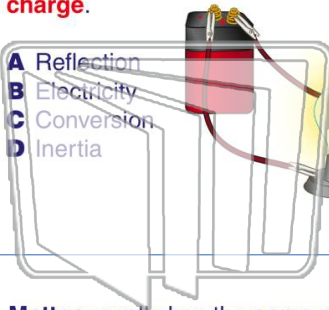- A Reflection
- B Electricity
- C Conversion
- D Inertia



2 \_\_\_\_\_ are made of **three different particles**. Some have a positive charge, some have a negative charge, and some have no charge at all.

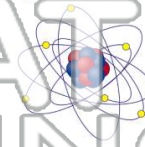- A Gases
- B Liquids
- C Solids
- D Atoms



3 **Matter** usually has the **same** number of positive and negative charges, making it **neutral**. If something had a charge of **-5**,

4 The **imbalance** of positive or negative charges **between** objects is called \_\_\_\_\_.




## PREVIEW

Please [Sign In](#) or [Sign Up](#) to download the printable version of this worksheet

7 \_\_\_\_\_ purpose of the **battery**?

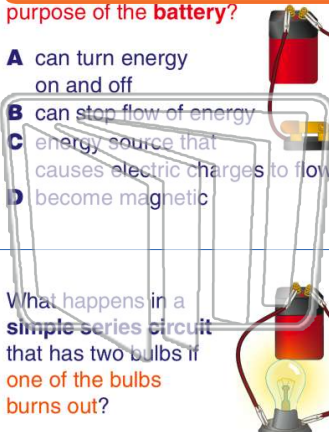- A can turn energy on and off
- B can stop flow of energy
- C energy source that causes electric charges to flow
- D become magnetic



8 \_\_\_\_\_ charge flows \_\_\_\_\_.

- A in two paths
- B in only one path
- C faster than parallel
- D backwards



9 What happens in a **simple series circuit** that has two bulbs if **one of the bulbs burns out**?

- A the other bulb will burn dimmer
- B the other bulb will burn brighter
- C the other bulb will stay lit
- D the other bulb will go out too



10 A(n) \_\_\_\_\_ circuit has **two or more paths** the electric charge can flow through.

- A parallel
- B series
- C open
- D closed

